
Logic and Computer Design Fundamentals

Chapter 5 – Registers and Register Transfers

Charles Kime & Thomas Kaminski

© 2004 Pearson Education, Inc.

[Terms of Use](#)


(Hyperlinks are active in View Show mode)

Registers


- **Register – a collection of binary storage elements**
- **In theory, a register is sequential logic which can be defined by a state table**
- **More often think of a register as storing a vector of binary values**
- **Frequently used to perform simple data storage and data movement and processing operations**

4-Bit Register

 - $\overline{\text{Clear}}$ goes to \overline{R}
- We put '1' all the time
- Put '0' if want to clear the values



(b) Symbol

 

Register with Parallel Load


- If data is not changed no need to trigger the clock
- Clock inputs = C inputs

$$C \text{ inputs} = \overline{\text{Load}} + \text{Clock}$$



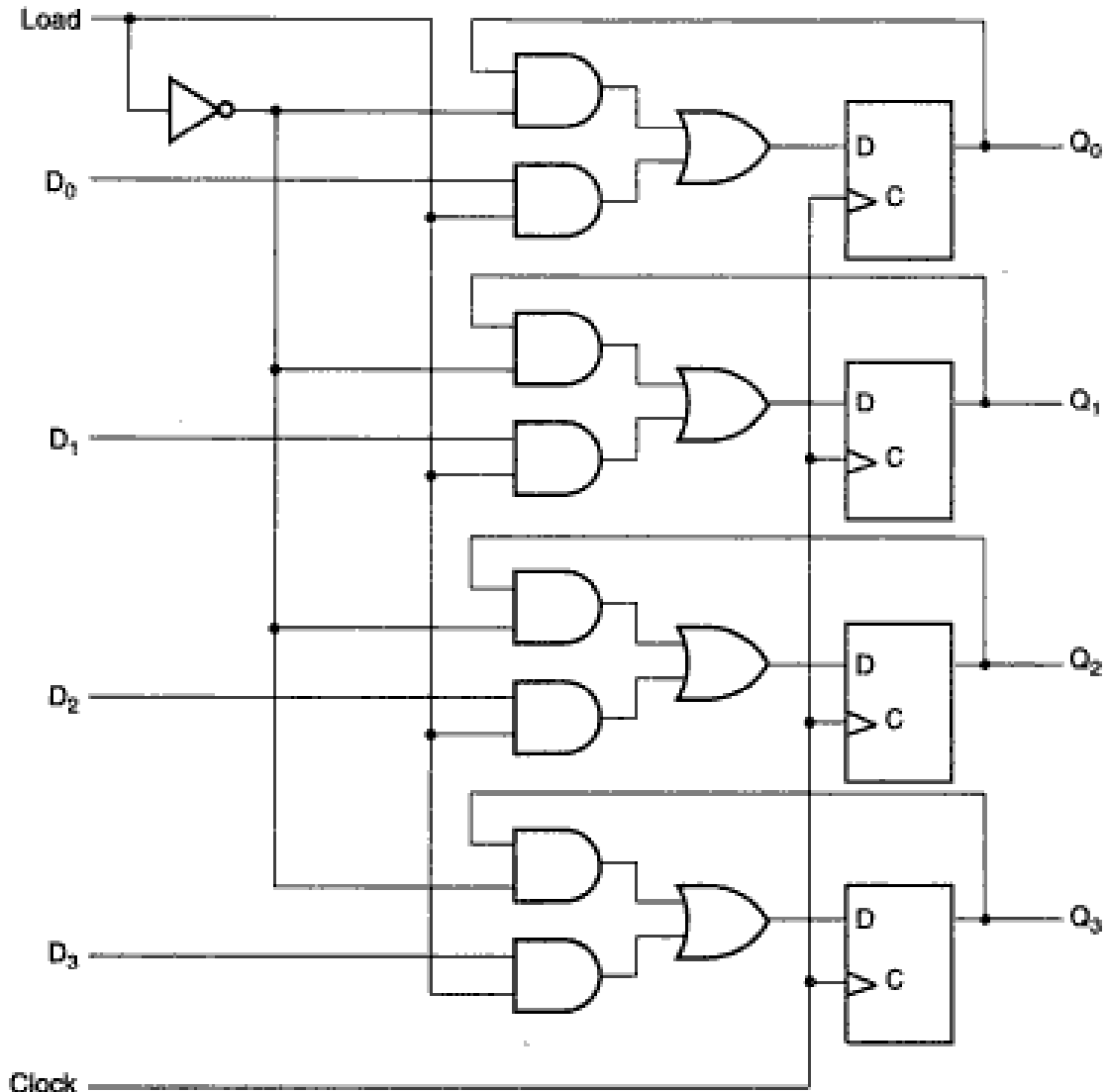
(c) Load control input

- When Load = 1, register clocked normally, new data is loaded
- Note, clock pulses arrive periodically, Load determines if new data would be loaded or not



Shift Registers

 
- Shift Registers move data laterally within the register toward its MSB or LSB position
- In the simplest case, the shift register is simply a set of D flip-flops connected in a row like this:



- Data input, In, is called a *serial input* or the *shift right input*.
- Data output, Out, is often called the *serial output*.
- The vector (A, B, C, Out) is called the *parallel output*.

Shift Registers (continued)

 - The behavior of the serial shift register is given in the listing on the lower right
- T0 is the register state just before the first clock pulse occurs
- T1 is after the first pulse and before the second.
- Initially unknown states are denoted by “?”
- Complete the last three rows of the table



CP	In	A	B	C	Out
T0	0	?	?	?	?
T1	1	0	?	?	?
T2	1	1	0	?	?
T3	0	1	1	0	?
T4	1				
T5	1				
T6	1				

Parallel Load Shift Registers

- By adding a mux between each shift register stage, data can be shifted or loaded
- If SHIFT is low, A and B are replaced by the data on D_A and D_B lines, else data shifts right on each clock.
- By adding more bits, we can make n -bit parallel load shift registers.
- A parallel load shift register with an added “hold” operation that stores data unchanged is given in Figure 7-10 of the text.

