

---

# Logic and Computer Design Fundamentals

## Chapter 5 – Counters

**Charles Kime & Thomas Kaminski**

© 2004 Pearson Education, Inc.

Terms of Use

(Hyperlinks are active in View Show mode)



# Counters

---

- **Counters** are sequential circuits which "count" through a specific state sequence. They can count up, count down, or count through other fixed sequences. Two distinct types are in common usage:
- **Ripple Counters**
  - Clock is connected to the flip-flop clock input on the LSB bit flip-flop
  - For all other bits, a flip-flop output is connected to the clock input, thus circuit is not truly synchronous
  - Output change is delayed more for each bit toward the MSB.
  - Resurgent because of low power consumption
- **Synchronous Counters**
  - Clock is directly connected to the flip-flop clock inputs
  - Logic is used to implement the desired state sequencing
  
# Ripple Counter

- **How does it work?**
  - When there is a positive edge on the clock input of A, A complements
  - The clock input for flip-flop B is the complemented output of flip-flop A
  - When flip A changes from 1 to 0, there is a positive edge on the clock input of B causing B to complement




# Ripple Counter (continued)

---

- These circuits are called *ripple counters* because each edge sensitive transition (positive in the example) causes a change in the next flip-flop's state.
- The changes “ripple” upward through the chain of flip-flops, i. e., each transition occurs after a clock-to-output delay from the stage before.
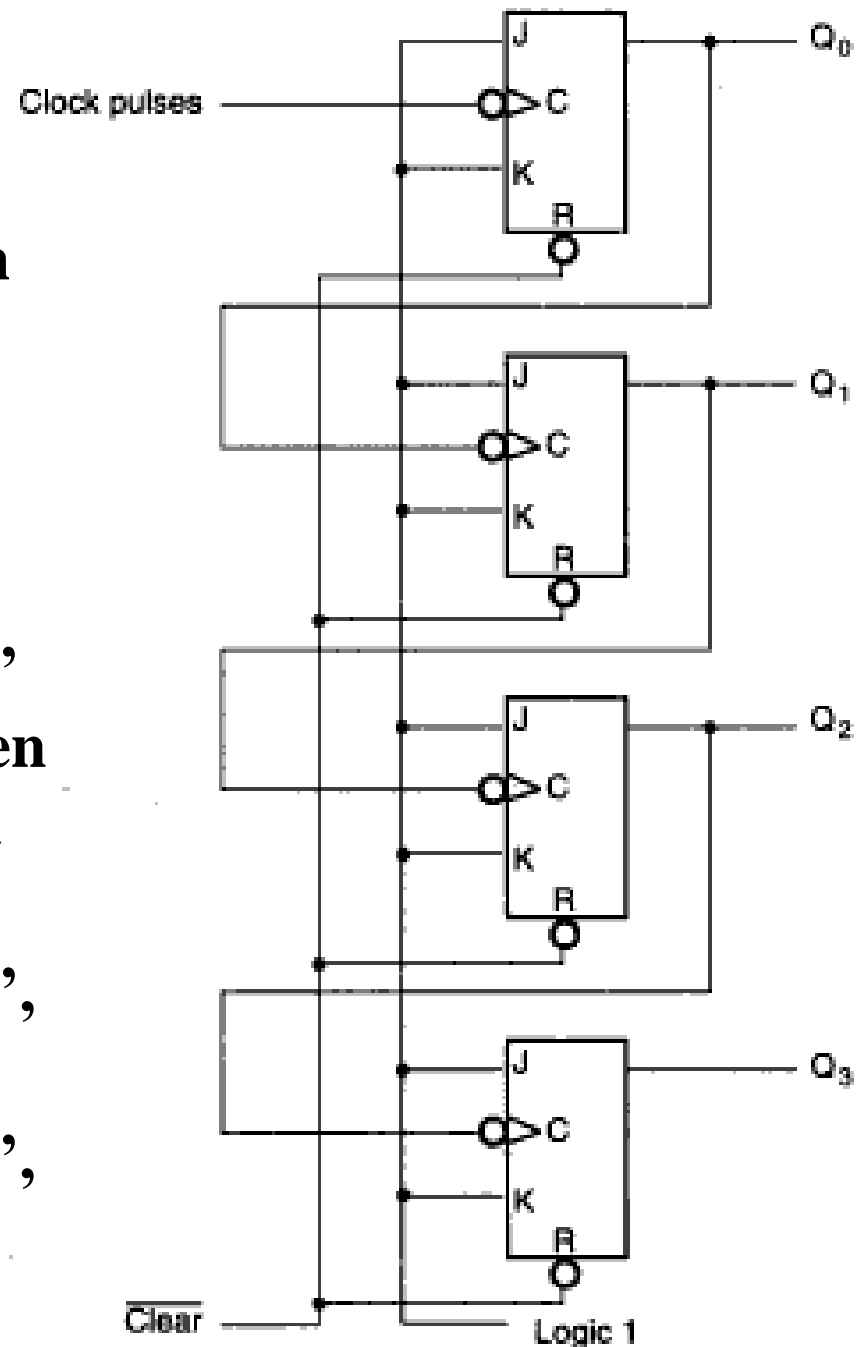
# Ripple Counter: 4-bit Upward Counter

- Remember J-K toggles when both J and K are '1'
- The bubble on the clock means negative-edge triggered
- When Q<sub>0</sub> goes from '1' to '0' (as if a negative-edge has been triggered to clock of Q<sub>1</sub>), Q<sub>1</sub> toggles
- When Q<sub>1</sub> goes from '1' to '0', Q<sub>2</sub> toggles
- When Q<sub>2</sub> goes from '1' to '0', Q<sub>3</sub> toggles



# Ripple Counter: 4-bit Upward Counter


- When Q0 goes from '1' to '0' (as if a negative-edge has been triggered to clock of Q1), Q1 toggles
- When Q1 goes from '1' to '0', Q2 toggles
- When Q2 goes from '1' to '0', Q3 toggles
- What about the last sequence: how it goes from '1111' to '0000'?

**Upward Counting Sequence**

<b>Q<sub>3</sub></b>	<b>Q<sub>2</sub></b>	<b>Q<sub>1</sub></b>	<b>Q<sub>0</sub></b>
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1
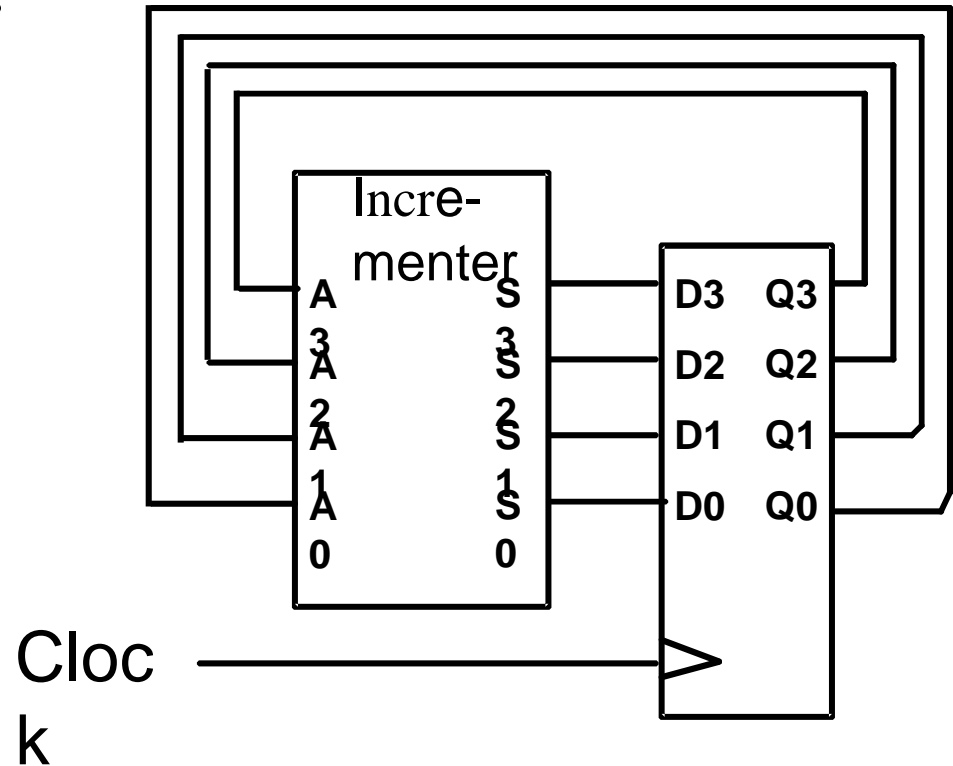
# Synchronous Counters

- To eliminate the "ripple" effects, use a common clock for each flip-flop and a combinational circuit to generate the next state.
- For an up-counter, use an incrementer =>



# 4-bit Synchronous Counter with J-K

(a) JK Flip-Flop			
$Q(t)$	$Q(t+1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Present state				Next state				Flip-flop inputs							
$Q_3$	$Q_2$	$Q_1$	$Q_0$	$Q_3$	$Q_2$	$Q_1$	$Q_0$	$J_{Q3}$	$K_{Q3}$	$J_{Q2}$	$K_{Q2}$	$J_{Q1}$	$K_{Q1}$	$J_{Q0}$	$K_{Q0}$
0	0	0	0	0	0	0	1	0	X	0	X	0	X	1	X
0	0	0	1	0	0	1	0	0	X	0	X	1	X	X	1
0	0	1	0	0	0	1	1	0	X	0	X	X	0	1	X
0	0	1	1	0	1	0	0	0	X	1	X	X	1	X	1
0	1	0	0	0	1	0	1	0	X	X	0	0	X	1	X
0	1	0	1	0	1	1	0	0	X	X	0	1	X	X	1
0	1	1	0	0	1	1	1	0	X	X	0	X	0	1	X
0	1	1	1	1	0	0	0	1	X	X	1	X	1	X	1
1	0	0	0	1	0	0	1	X	0	0	X	0	X	1	X
1	0	0	1	1	0	1	0	X	0	0	X	1	X	X	1
1	0	1	0	1	0	1	1	X	0	0	X	X	0	1	X
1	0	1	1	1	1	0	0	X	0	1	X	X	1	X	1
1	1	0	0	1	1	0	1	X	0	X	0	0	X	1	X
1	1	0	1	1	1	1	0	X	0	X	0	1	X	X	1
1	1	1	0	1	1	1	1	X	0	X	0	X	0	1	X
1	1	1	1	0	0	0	0	X	1	X	1	X	1	X	1



# K-Maps

$Q_1Q_0$		$Q_1$			
$Q_3Q_2$		00	01	11	10
00					
01				1	
11	X	X	X	X	X
10	X	X	X	X	X

$Q_0$

$Q_2$

$$J_{Q3} = Q_0Q_1Q_2$$

X	X	X	X
X	X	X	X
		1	

$$K_{Q3} = Q_0Q_1Q_2$$

	1	X	X
	1	X	X
	1	X	X
	1	X	X

$$J_{Q1} = Q_0$$

		1	
X	X	X	X
X	X	X	X
		1	

$$J_{Q2} = Q_0Q_1$$

X	X	X	X
		1	
		1	
X	X	X	X

$$K_{Q2} = Q_0Q_1$$

X	X	1	
X	X	1	
X	X	1	
X	X	1	

$$K_{Q1} = Q_0$$

# Equations

---

- EN has been added to control the operation of the counter

$$J_{Q0} = K_{Q0} = EN$$

$$J_{Q1} = K_{Q1} = Q_0 \cdot EN$$

$$J_{Q2} = K_{Q2} = Q_0 \cdot Q_1 \cdot EN$$



$$J_{Q3} = K_{Q3} = Q_0 \cdot Q_1 \cdot Q_2 \cdot EN$$

- This relations could be generalized

$$J_{Qi} = K_{Qi} = Q_0 \cdot Q_1 \cdot Q_2 \cdot \dots \cdot Q_{i-1} \cdot EN$$

- A Carry Output (CO) has been added so that the counter could be extended to more stages
- The implementation might be positive/negative edge triggered

# Logic Diagram

 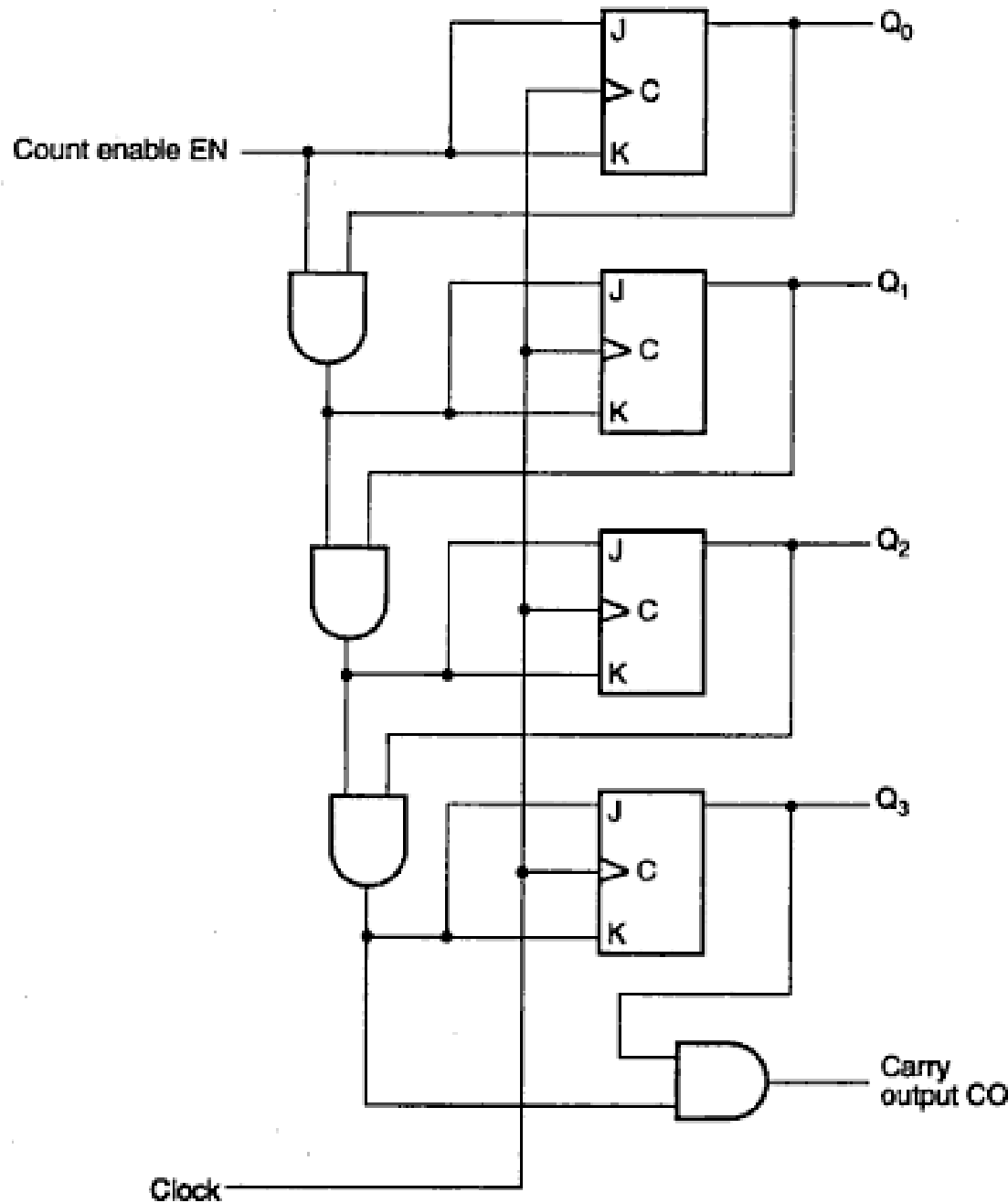

(b) Symbol


# Arbitrary Counter: Problem Statement

---

- Design an arbitrary counter that repeatedly follows the following sequence:  
**0, 1, 2, 4, 5, 6, 0, 1, 2, 4, 5, 6, 0...**

# Arbitrary Counter: State Diagram

---

 

(b) State diagram

# Arbitrary Counter: State Table

□ **TABLE 5-8**  
**State Table and Flip-Flop Inputs for Counter**

Present State			Next State			Flip-Flop Inputs					
A	B	C	A	B	C	J <sub>A</sub>	K <sub>A</sub>	J <sub>B</sub>	K <sub>B</sub>	J <sub>C</sub>	K <sub>C</sub>
0	0	0	0	0	1	0	×	0	×	1	×
0	0	1	0	1	0	0	×	1	×	×	1
0	1	0	1	0	0	1	×	×	1	0	×
1	0	0	1	0	1	×	0	0	×	1	×
1	0	1	1	1	0	×	0	1	×	×	1
1	1	0	0	0	0	×	1	×	1	0	×

$$J_A = B$$

$$K_A = B$$

$$J_B = C$$

$$K_B = 1$$


$$J_C = \overline{B}$$

$$K_C = 1$$

**Flip-Flop Excitation Tables**

(a) JK Flip-Flop			
Q(t)	Q(t + 1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

# Arbitrary Counter: Logic Diagram

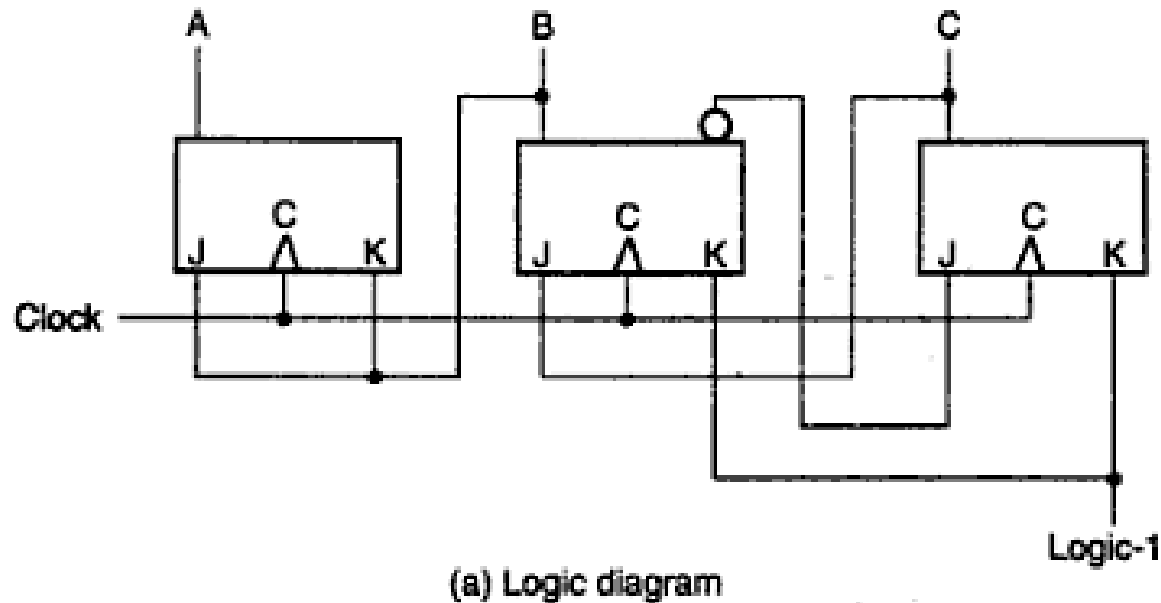

$$\begin{array}{ll} J_A = B & K_A = B \\ J_B = C & K_B = 1 \\ J_C = \overline{B} & K_C = 1 \end{array}$$